
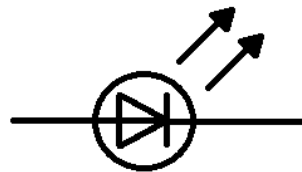
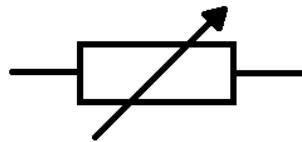


Paper 1

Chapter 2 — Electricity

Label Circuit Symbols

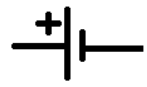

Draw Circuit Symbols

Lamp

Fuse


Voltmeter

Ammeter

Thermistor

LDR

Draw the IV Characteristic

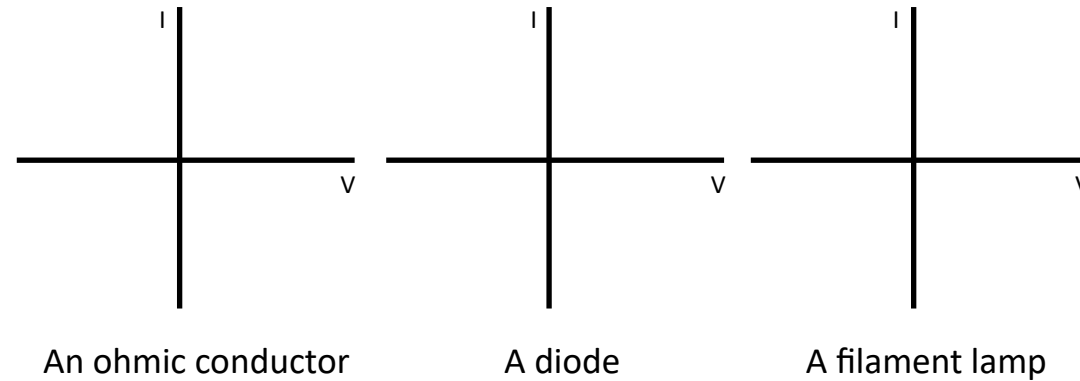


Calculation Practice

1.) If a 100W bulb has a current of 2A what is its resistance?

Resistance = ____ ()

2.) How much energy will a 100W bulb transfer if left on for 5 minutes?

Energy transferred = ____ ()

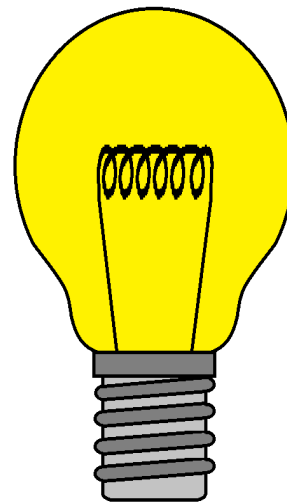

3 Core Cable

Label the wires and give the potential difference between each wire and earth.



Thermistor and LDR


The resistance of a thermistor _____ as the temperature increases.

A thermistor could be used to...

The resistance of an LDR _____ as light intensity increases.

A LDR could be used to...



$V = I \times R$

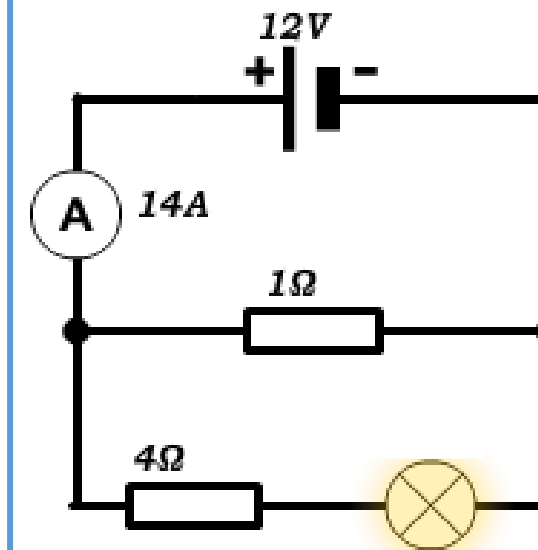

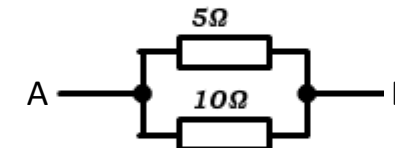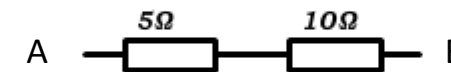- 1.) What is the potential difference across the 1Ω resistor?
- 2.) What is the current through the 1Ω resistor?
- 3.) What is the current through the bulb?
- 4.) What is the total resistance for the bottom path?
- 5.) What is the resistance of the bulb?

Resistance

What is the resistance between A and B in each picture?



Complete the Equations

(include units)

charge flow (C) =

potential difference (V) =

power (W) = potential difference (V) ×

power (W) = current (A) ² ×

energy transferred (J) = power (W) ×

energy transferred (J) = charge flow (C) ×

National Grid

The National Grid is made up of c_____ and t_____ linking p_____ s_____ to consumers.

Step _____ transformers are used to _____ the potential difference for the transmission cables then step _____ transformers are used to _____ the potential difference for consumers.

Mains Electricity


Mains electricity supplies an a_____ c_____.

In the UK the mains supply has a frequency of _____ and is about _____ V.


Paper 1

Chapter 2 — Electricity


Label Circuit Symbols

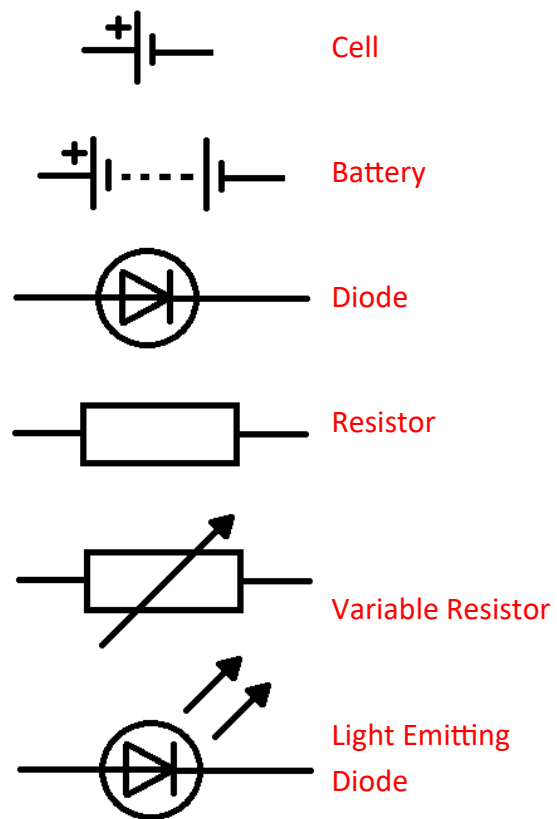

Draw Circuit Symbols

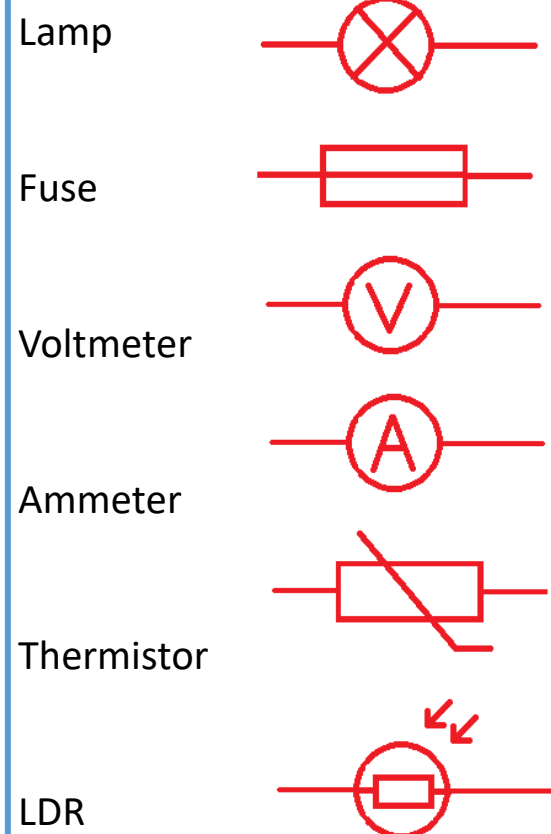

Draw the IV Characteristic

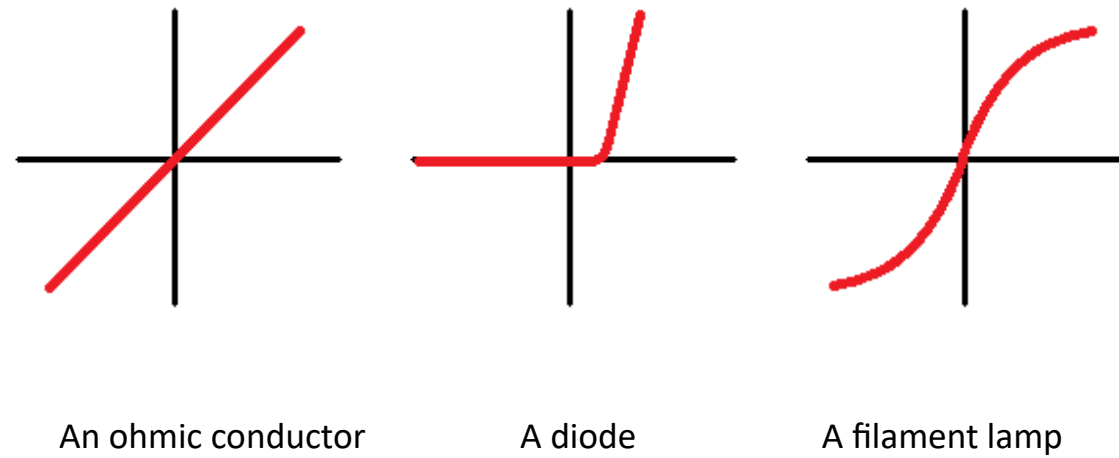

Calculation Practice

1.) If a 100W bulb has a current of 2A what is its resistance? $\text{power} = \text{current}^2 \times \text{resistance}$

$$100 = 2^2 \times \text{resistance} \quad 100/4 = \text{resistance} = 25$$


$$\text{Resistance} = 25\Omega$$

2.) How much energy will a 100W bulb transfer if left on for 5 minutes?

$$\text{Energy transferred} = \text{power} \times \text{time}$$


$$= 100\text{W} \times 300\text{s} = 30,000$$
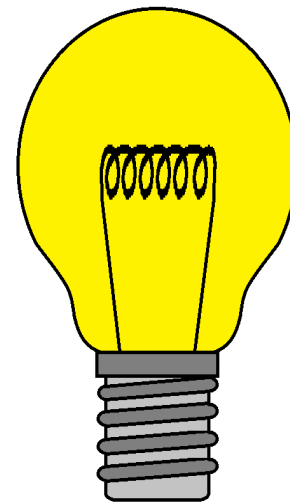
$$\text{Energy transferred} = 30,000\text{J}$$



3 Core Cable

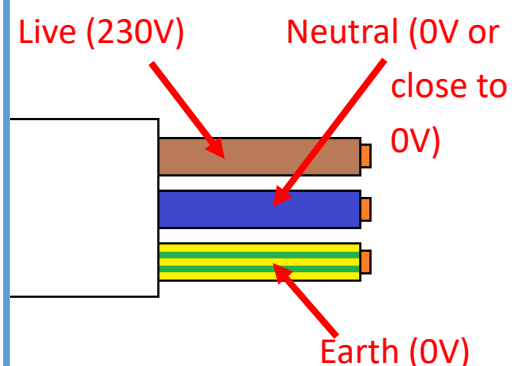Label the wires and give the potential difference between each wire and earth.



Thermistor and LDR


The resistance of a thermistor **decreases** as the temperature increases.

A thermistor could be used to... **make a thermostat keep a building at a certain temperature.**

The resistance of an LDR **decreases** as light intensity increases.

A LDR could be used to... **switch on lights when it gets dark.**



$V = I \times R$

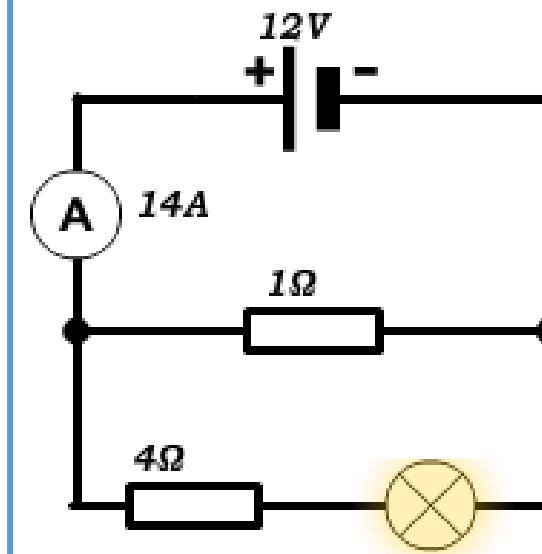

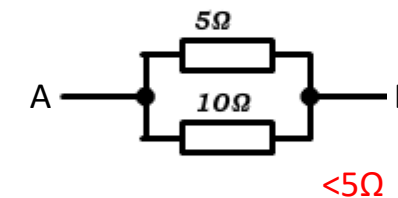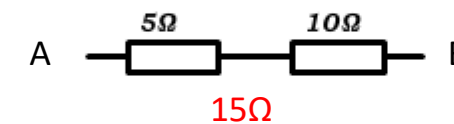- 1.) What is the potential difference across the 1Ω resistor? **12V**
- 2.) What is the current through the 1Ω resistor? **12A**
- 3.) What is the current through the bulb? **2A**
- 4.) What is the total resistance for the bottom path? **6Ω**
- 5.) What is the resistance of the bulb? **2Ω**

Resistance

What is the resistance between A and B in each picture?



Complete the Equations

(include units)

$$\text{charge flow (C)} = \text{current (A)} \times \text{time (s)}$$

$$\text{potential difference (V)} = \text{current (A)} \times \text{resistance (}\Omega\text{)}$$

$$\text{power (W)} = \text{potential difference (V)} \times \text{current (A)}$$

$$\text{power (W)} = \text{current (A)}^2 \times \text{resistance (}\Omega\text{)}$$

$$\text{energy transferred (J)} = \text{power (W)} \times \text{time (s)}$$

$$\text{energy transferred (J)} = \text{charge flow (C)} \times \text{potential difference (V)}$$

National Grid

The National Grid is made up of **cables** and **transformers** linking **power stations** to consumers.

Step **up** transformers are used to **increase** the potential difference for the transmission cables then step **down** transformers are used to **decrease** the potential difference for consumers.

Mains Electricity

Mains electricity supplies an **alternating current**.

In the UK the mains supply has a frequency of **50Hz** and is about **230 V**.